

Worksheet of the student

Date of Performance: 30/1/2015

Registration No: 11206693


Exp.No:2

Roll No: E1206 A15


Aim: mplementation of full adder/subtracter and half adder/subtracter using Verilog in Xilinx Tool

Attach Graph/Simulation Waveforms:


1-full adder

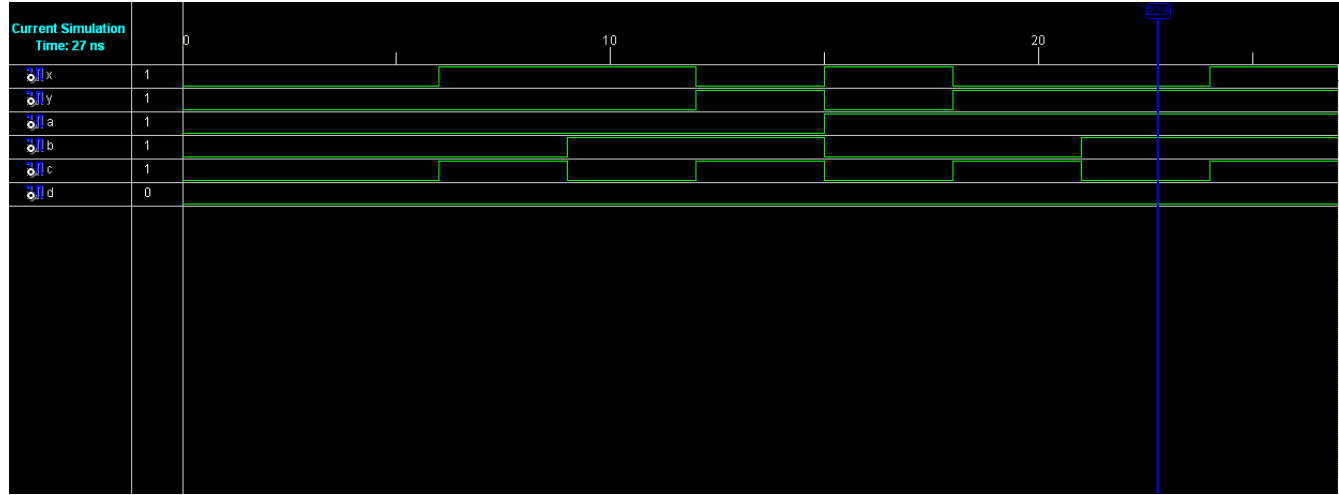


2-full subtracter

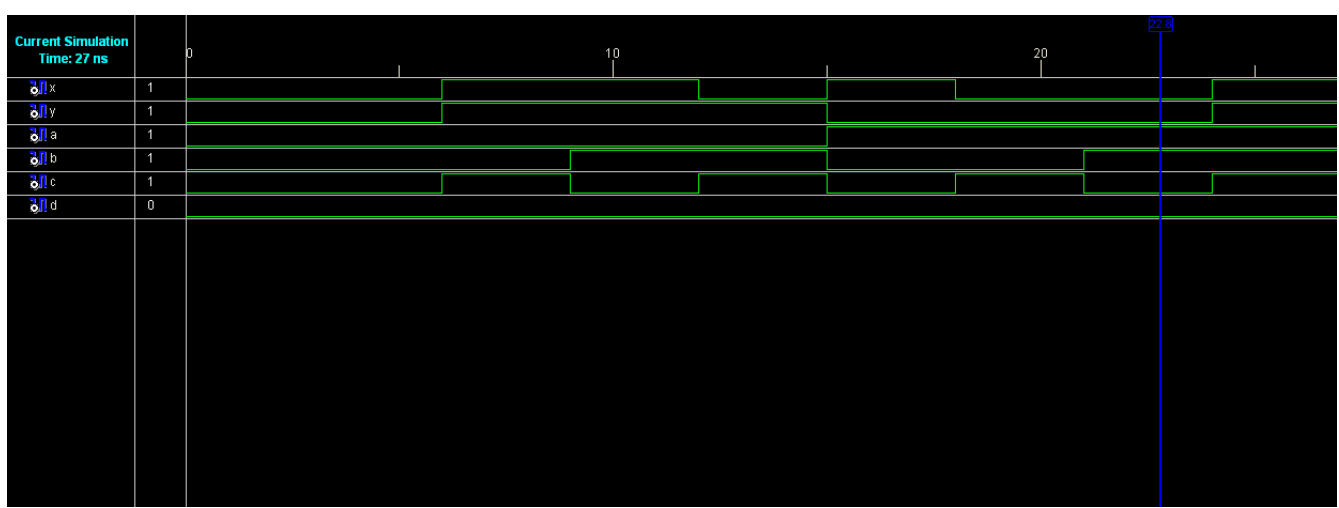

3-half adder

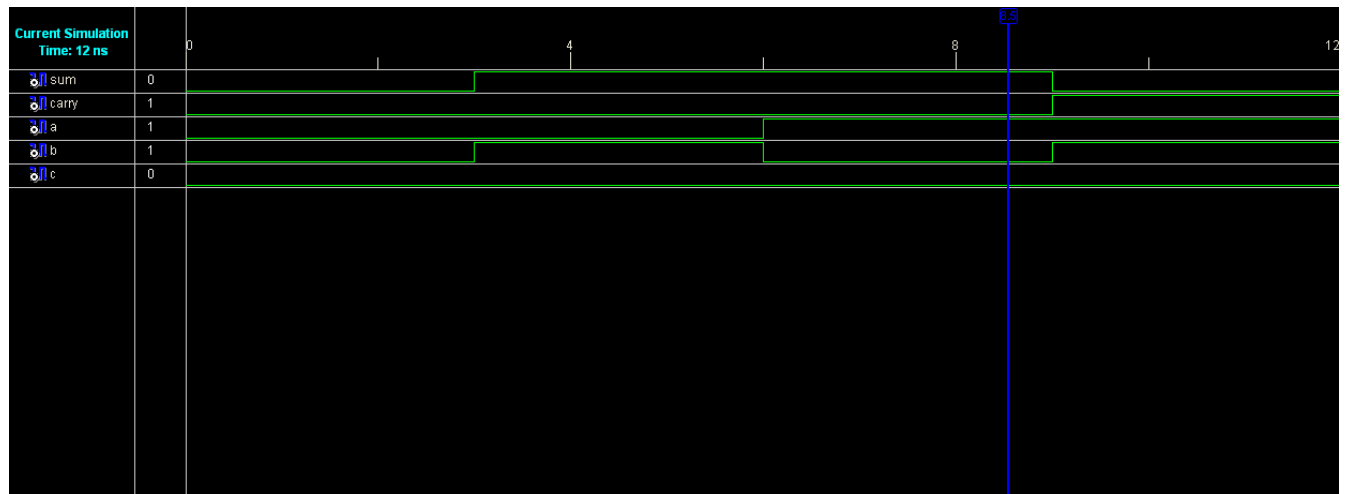

4-half subtractor

 

Program code:

1-full adder:

```
module full(a,b,c,d, x,y);  
  input a,b,c,d;  
  output x,y;  
  assign x=(a^b^c);  
  assign y=(a&b)|(b&c)|(c&a);
```

endmodule

2-full subtractor

```
module fullsub(a,b,c,d, x,y);  
  input a,b,c,d;  
  output x,y;  
  assign x=(a^b^c);  
  assign y=((~a)&b)|(b&c)|(c&(~a));  
endmodule
```

3-half adder:

```
module halfadder(a,b,c, sum,carry);  
    input a,b,c;  
    output sum,carry;  
    assign sum=(a^b);  
    assign carry=(a&b);
```

endmodule

4-half subtractor:

```
module halfsub(a,b,c, diff,bor);  
    input a,b,c;  
    output diff,bor;  
    assign diff=(a^b);  
    assign bor=(a&b);
```

endmodule

Testbench:

1-full adder:

```
module fullt_v;  
  
    // Inputs  
    reg a;  
    reg b;  
    reg c;  
    reg d;  
  
    // Outputs  
    wire x;  
    wire y;  
  
    // Instantiate the Unit Under Test (UUT)  
    full uut (  
        .a(a),  
        .b(b),  
        .c(c),  
        .d(d),  
        .x(x),  
        .y(y)  
    );  
  
    initial begin  
        // Initialize Inputs  
        a = 0;  
        b = 0;  
        c = 0;  
        d = 0;  
        #3 a=0;b=0;c=0;  
        #3 a=0;b=0;c=1;
```

```
#3 a=0;b=1;c=0;
    #3 a=0;b=1;c=1;
    #3 a=1;b=0;c=0;
    #3 a=1;b=0;c=1;
    #3 a=1;b=1;c=0;
    #3 a=1;b=1;c=1;
    #3 $stop;
```

end

endmodule

2-full subtractor:

module fullsubt_v;

// Inputs

reg a;

reg b;

reg c;

reg d;

// Outputs

wire x;

wire y;

// Instantiate the Unit Under Test (UUT)

fullsub uut (

.a(a),

.b(b),

.c(c),

.d(d),

.x(x),

.y(y)

);

initial begin

// Initialize Inputs

a = 0;

b = 0;

c = 0;

d = 0;

#3 a=0;b=0;c=0;

#3 a=0;b=0;c=1;

#3 a=0;b=1;c=0;

#3 a=0;b=1;c=1;

#3 a=1;b=0;c=0;

#3 a=1;b=0;c=1;

#3 a=1;b=1;c=0;

#3 a=1;b=1;c=1;

```

        #3 $stop;
    end

endmodule
3-half adder:
module halfat_v;

    // Inputs
    reg a;
    reg b;
    reg c;

    // Outputs
    wire sum;
    wire carry;

    // Instantiate the Unit Under Test (UUT)
    halfadder uut (
        .a(a),
        .b(b),
        .c(c),
        .sum(sum),
        .carry(carry)
    );

    initial begin
        // Initialize Inputs
        a = 0;
        b = 0;
        c = 0;

        #3 a=0;b=1;
        #3 a=1; b=0;
        #3 a=1; b=1;
        #3 $stop;
    end

endmodule
4-half subtractor:
module halfsubt_v;

    // Inputs
    reg a;
    reg b;
    reg c;

    // Outputs
    wire diff;
    wire bor;

```

```
// Instantiate the Unit Under Test (UUT)
```

```
halfsub uut (  
    .a(a),  
    .b(b),  
    .c(c),  
    .diff(diff),  
    .bor(bor)  
);
```

```
initial begin  
    // Initialize Inputs  
    a = 0;  
    b = 0;  
    c = 0;  
  
    #3 a=0;b=1;  
    #3 a=1; b=0;  
    #3 a=1; b=1;  
    #3 $stop;  
end
```

```
endmodule
```

Console window output:

1-full adder

Started : "Check Syntax".

Running vlogcomp

Compiling project file "fullt_v_stx.prj"

Compiling verilog file "D:/New Folder/anubhav/full adder.v" in library isim_temp

Module <full> compiled

Parsing D:/New Folder/anubhav/full adder.v: 0.02

Compiling verilog file "D:/New Folder/anubhav/fullt.v" in library isim_temp

Module <fullt_v> compiled

Parsing D:/New Folder/anubhav/fullt.v: 0.01

Compiling verilog file "C:/Xilinx92i/verilog/src/glbl.v" in library isim_temp

Module <glbl> compiled

Parsing C:/Xilinx92i/verilog/src/glbl.v: 0.02

Process "Check Syntax" successful

2-full subtractor:

Started : "Check Syntax".

Running vlogcomp

Compiling project file "fullsubt_v_stx.prj"

Compiling verilog file "D:/New Folder/anubhav/fullsub.v" in library isim_temp

Module <fullsub> compiled

Parsing D:/New Folder/anubhav/fullsub.v: 0.02

Compiling verilog file "D:/New Folder/anubhav/fullsubt.v" in library isim_temp

Module <fullsubt_v> compiled
Parsing D:/New Folder/anubhav/fullsubt.v: 0.01
Compiling verilog file "C:/Xilinx92i/verilog/src/glbl.v" in library isim_temp
Module <glbl> compiled
Parsing C:/Xilinx92i/verilog/src/glbl.v: 0.02



Process "Check Syntax" successful
3-half adder:



Started : "Check Syntax".
Running vlogcomp
Compiling project file "halfat_v_stx.prj"
Compiling verilog file "D:/New Folder/anubhav/halfadder.v" in library isim_temp
Module <halfadder> compiled
Parsing D:/New Folder/anubhav/halfadder.v: 0.01
Compiling verilog file "D:/New Folder/anubhav/halfat.v" in library isim_temp
Module <halfat_v> compiled
Parsing D:/New Folder/anubhav/halfat.v: 0.03
Compiling verilog file "C:/Xilinx92i/verilog/src/glbl.v" in library isim_temp
Module <glbl> compiled
Parsing C:/Xilinx92i/verilog/src/glbl.v: 0.01

Process "Check Syntax" successful
4-half subtractor:

Started : "Check Syntax".
Running vlogcomp
Compiling project file "halfsubt_v_stx.prj"
Compiling verilog file "D:/New Folder/anubhav/halfsub.v" in library isim_temp
Module <halfsub> compiled
Parsing D:/New Folder/anubhav/halfsub.v: 0.03
Compiling verilog file "D:/New Folder/anubhav/halfsubt.v" in library isim_temp
Module <halfsubt_v> compiled
Parsing D:/New Folder/anubhav/halfsubt.v: 0.02
Compiling verilog file "C:/Xilinx92i/verilog/src/glbl.v" in library isim_temp
Module <glbl> compiled
Parsing C:/Xilinx92i/verilog/src/glbl.v: 0.02

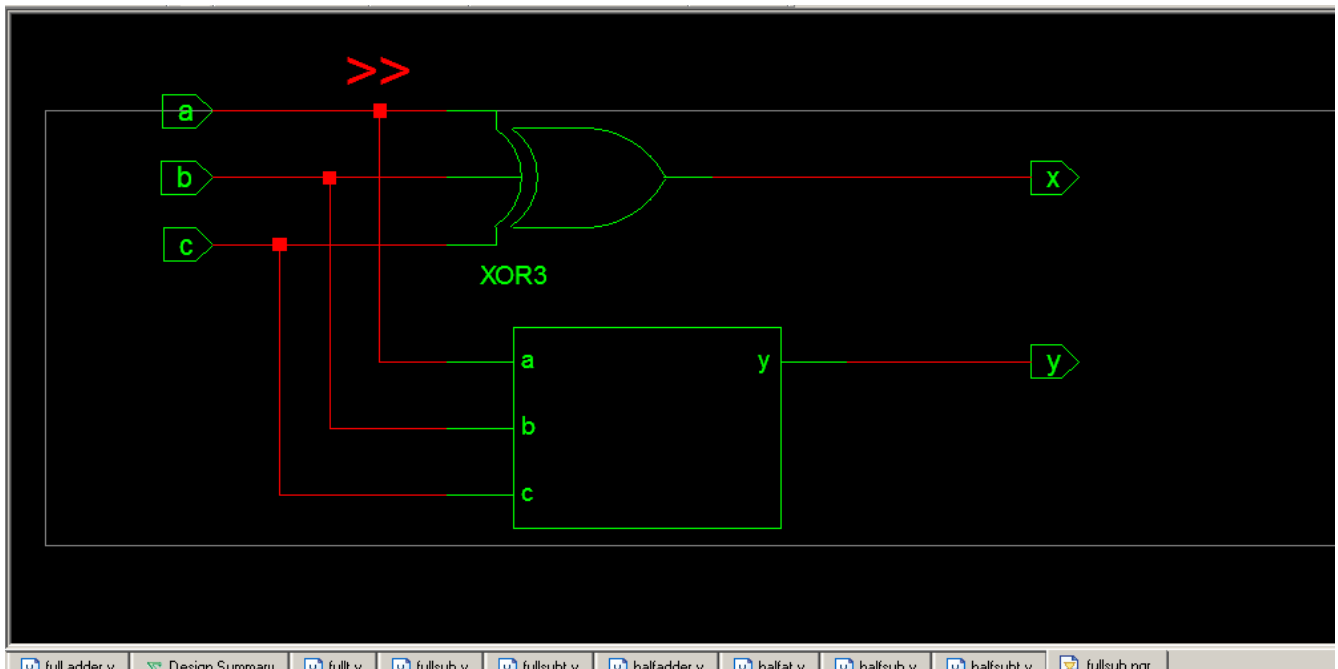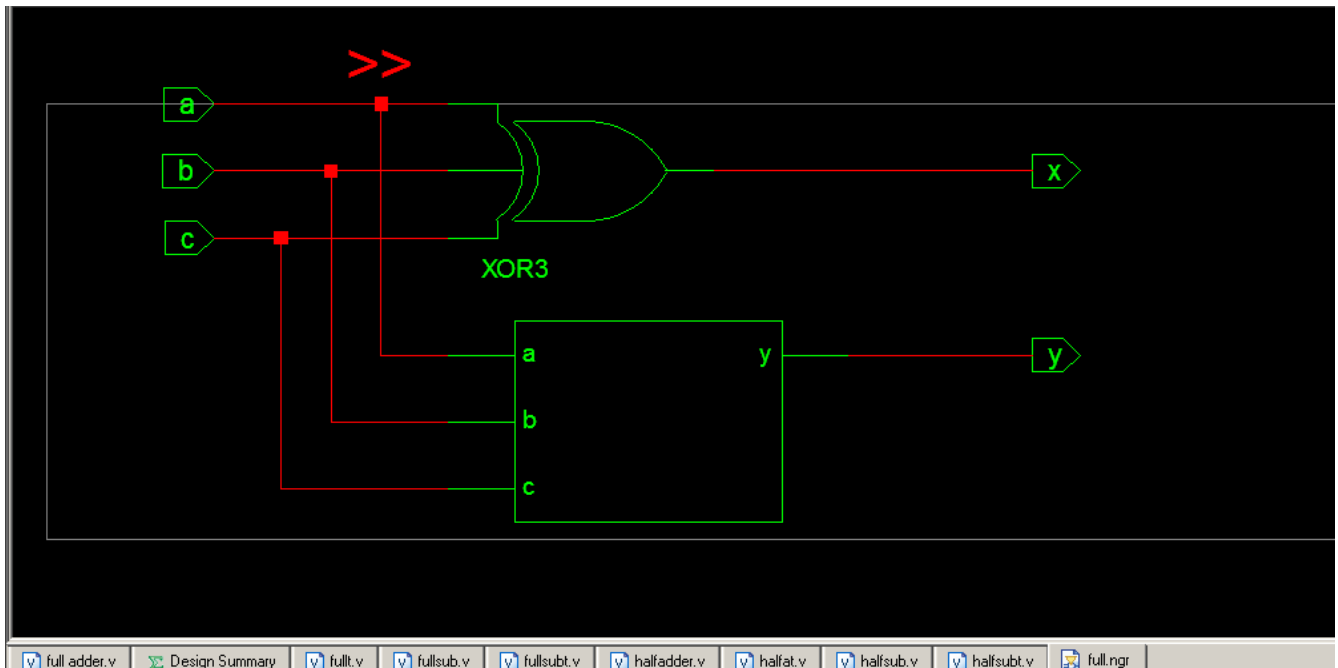Process "Check Syntax" successful
RTL Schematic output:
1-full adder:



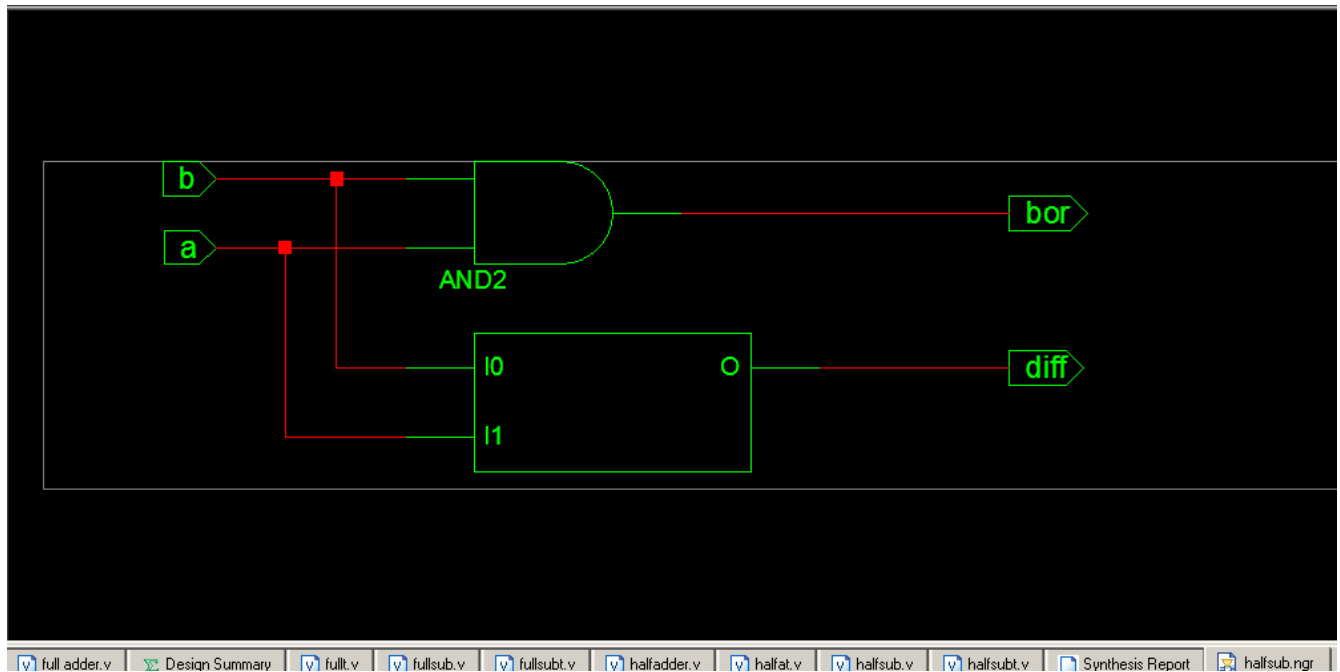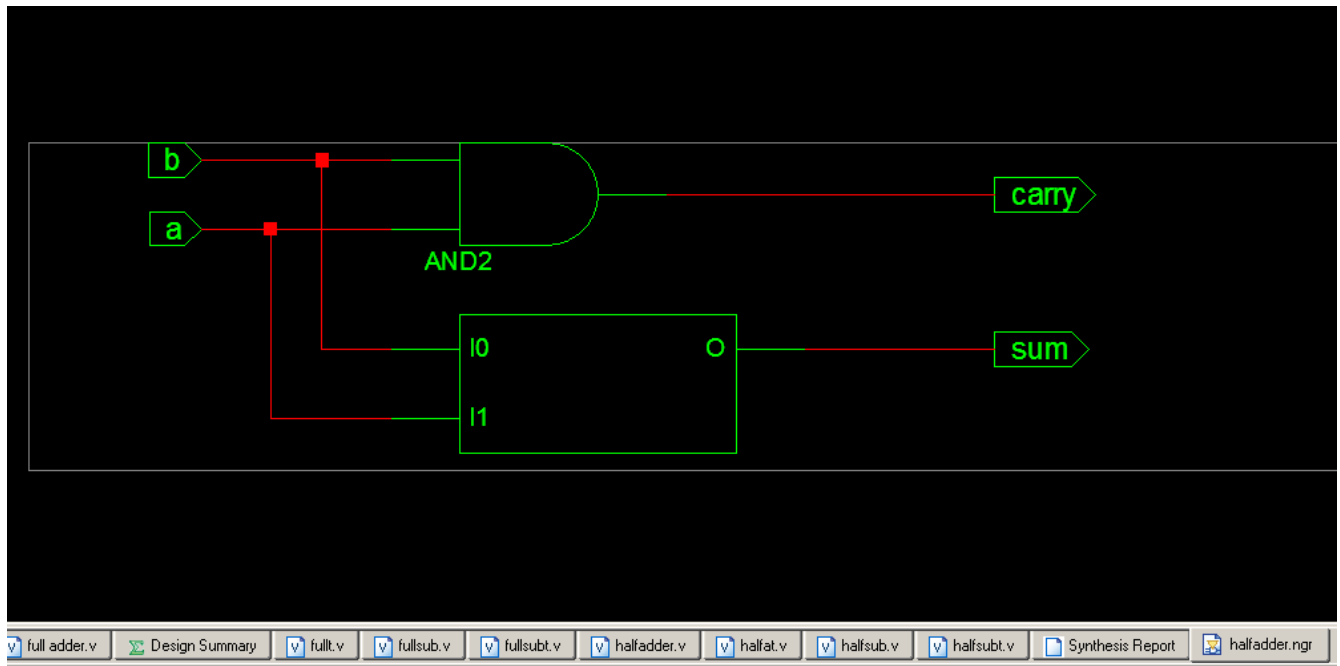

Result and Discussion:

All the adder and subtractor are successfully implemented using verilog language and verified in xilinx.

Learning Outcomes (what I have learnt):

from this experiment we have learned how to make full adder/subtractor halfadder/subtractor using xilinx software in verilog language.

To be filled by Faculty

S.No.	Parameter (Scale from 1-10, 1 for very poor and 10 excellent)	Max. Marks	Marks Obtained
1	Understanding of the student about the procedure/apparatus.		20
2	Observations and analysis including learning Outcomes		20
3	Completion* of experiment, Discipline and Cleanliness		10
4	Signature of Faculty Total marks Obtained	Total marks obtained	